
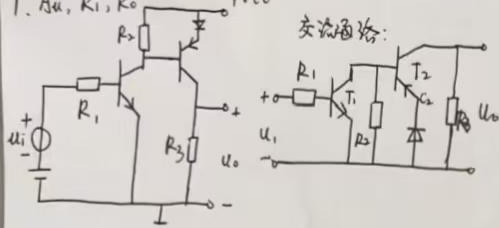



1. A_u, R_i, R_o

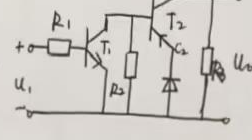

交流通路:



微变等效电路:

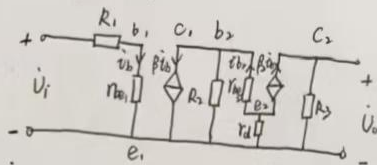

$$r_d = \frac{n U_T}{I_{DQ}}$$


$$A_{u1} = - \frac{\beta_1 R_2 // [r_{be2} + (1 + \beta_2) r_d]}{r_{be1} + R_1}$$

$$A_{u2} = - \frac{\beta_2 R_3}{r_{be2} + (1 + \beta_2) r_d}$$

$$A_u = A_{u1} \cdot A_{u2} = - \frac{\beta_1 \beta_2 R_2 R_3}{(r_{be1} + R_1) [r_{be2} + (1 + \beta_2) r_d]}$$


$$R_i = R_1 + r_{be1} \quad R_o = R_3$$

2.

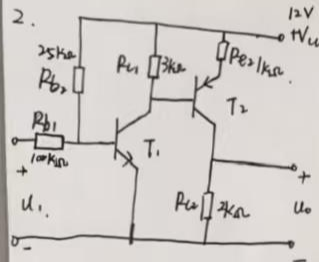


$\beta_1 = 80, r_{be1} = 1 \text{ k}\Omega, \beta_2 = 60, r_{be2} = 1 \text{ k}\Omega$

交流通路:

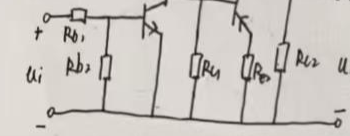

A_u, R_i, R_o

微变等效电路:

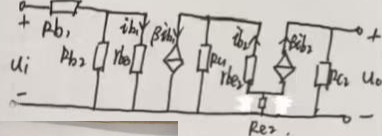

$$A_{u1} = - \frac{\beta_1 i_{b1} \{ R_2 // [r_{be2} + (1 + \beta_2) R_{L2}] \}}{r_{be1} i_{b1}} = - \frac{\beta_1 \{ R_2 // [r_{be2} + (1 + \beta_2) R_{L2}] \}}{r_{be1}}$$


$$A_{u2} = - \frac{\beta_2 i_{b2} R_{L2}}{i_{b2} [r_{be2} + (1 + \beta_2) R_{L2}]} = - \frac{\beta_2 R_{L2}}{r_{be2} + (1 + \beta_2) R_{L2}}$$

$$A_u = A_{u1} \cdot A_{u2} =$$


$$R_i = R_1 // (R_2 // r_{be1}) =$$

$$R_o = R_{L2} =$$

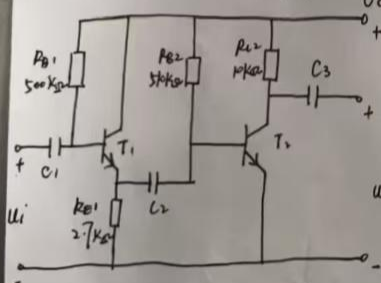
3. $\beta_1 = \beta_2 = 50, A_u, R_i, R_o$



交流通路:

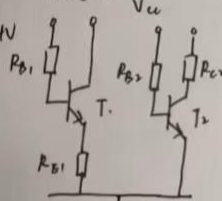

微变等效电路:

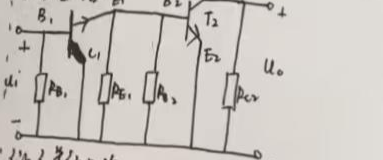

$$i_{B1} = \frac{V_{CC} - U_{CEQ1}}{R_{B1} + (1 + \beta_1) R_E} = 31.5 \mu\text{A}$$


$$U_{B2} = \frac{V_{CC} - U_{CEQ2}}{R_{B2} + (1 + \beta_2) R_E} = 4.5 \text{ V}$$

$$I_{EQ1} = (1 + \beta_1) I_{B1} = 1.6 \text{ mA}$$

$$r_{be1} = 300 \Omega + \frac{26 \text{ mV}}{I_{EQ1}} = 1 \text{ k}\Omega$$

$$r_{be2} = 668 \Omega$$

微变等效电路:

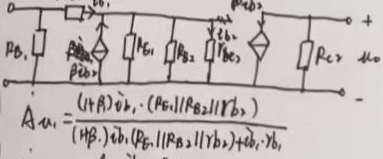

$$A_{u1} = \frac{(1 + \beta_1) i_{b1} \cdot (R_{B2} // R_{B3} // r_{be2})}{(1 + \beta_1) i_{b1} (R_{B1} // R_{B2} // r_{be1}) + i_{b1} r_{be1}}$$



$$A_{u2} = - \frac{\beta_2 i_{b2} R_{L2}}{i_{b2} r_{be2}}$$

$$A_u = A_{u1} \cdot A_{u2}$$

$$R_i = R_{B1} // [r_{be1} + (1 + \beta_1) (R_{B2} // R_{B3} // r_{be2})]$$

$$R_o = R_{L2}$$

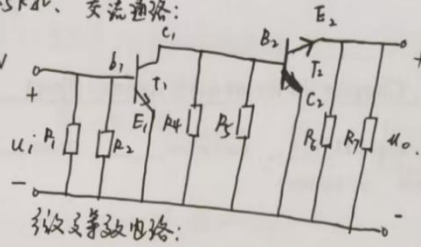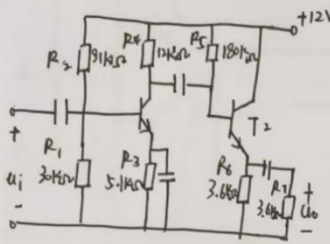4. $\beta_1 = \beta_2 = 100$, $r_{be1} = 6k\Omega$, $r_{be2} = 1.5k\Omega$. 交流通路:
 A_u , R_i , R_o .



交流通路:



$$A_{u1} = \frac{-\beta_1 I_{b1} \cdot (R_4 // R_5 // R_6 // R_7)}{I_{b1} \cdot r_{be1}}$$

$$A_{u2} = \frac{(1 + \beta_2) (R_6 // R_7) I_{b2}}{(1 + \beta_2) (R_6 // R_7) I_{b2} + r_{be2} \cdot I_{b2}}$$

$$A_u = A_{u1} \cdot A_{u2}$$

$$R_i = R_1 // R_2 // r_{be1}$$

$$R_o = R_4 // R_5 // R_6 // R_7$$

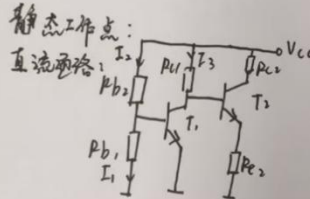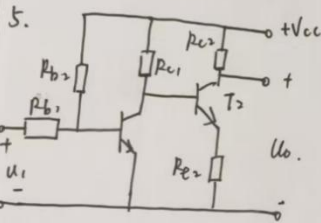

静态工作点:

$$V_{cc} = I_{b1} \cdot R_{b1} + I_{c1} \cdot R_{c1} + I_{b2} \cdot R_{b2} + I_{c2} \cdot R_{c2}$$

$$V_{cc} = I_{b1} \cdot R_{b1} + I_{c1} \cdot R_{c1} + I_{b2} \cdot R_{b2} + I_{c2} \cdot R_{c2}$$

$$\Rightarrow I_{b1} = \frac{V_{cc} - U_{BEQ1}}{R_{b1}} \quad I_{c1} = \beta_1 I_{b1}$$

$$I_{b2} = I_{c1} - I_{b1} = \frac{V_{cc} - U_{BEQ1}}{R_{b2}} - \frac{U_{BEQ1}}{R_{b1}}$$

$$I_{c2} = \beta_2 I_{b2} = \beta_2 \left(\frac{V_{cc} - U_{BEQ1}}{R_{b2}} - \frac{U_{BEQ1}}{R_{b1}} \right)$$

$$V_{cc} = I_{c1} R_{c1} + U_{BEQ1} + (1 + \beta_2) I_{b2} \cdot R_{c2}$$

$$\Rightarrow I_{b2} = I_{c1} - I_{b1} \Rightarrow I_{c1} = \frac{V_{cc} - U_{BEQ1} - (1 + \beta_2) I_{b2} \cdot R_{c2}}{R_{c1}}$$

$$\Rightarrow V_{cc} = I_{c1} \cdot R_{c1} + U_{BEQ1}$$

$$V_{cc} = I_{c1} R_{c1} + U_{BEQ1} + I_{e2} \cdot R_{e2}$$

$$I_{e2} = (1 + \beta_2) I_{b2}, \quad I_{c2} = \beta_2 I_{b2}$$

$$\Rightarrow I_{BQ1} = \frac{V_{cc} - U_{BEQ1}}{R_{b1}} - \frac{U_{BEQ1}}{R_{b1}}$$


$$I_{CQ1} = \beta_1 \left(\frac{V_{cc} - U_{BEQ1}}{R_{b1}} - \frac{U_{BEQ1}}{R_{b1}} \right)$$

$$U_{CEQ1} = V_{cc} - R_{c1} \cdot I_{C1} = \dots$$

$$I_{BQ2} = I_{c1} - I_{BQ1} = \dots$$

$$I_{CQ2} = \beta_2 I_{BQ2} = \dots$$
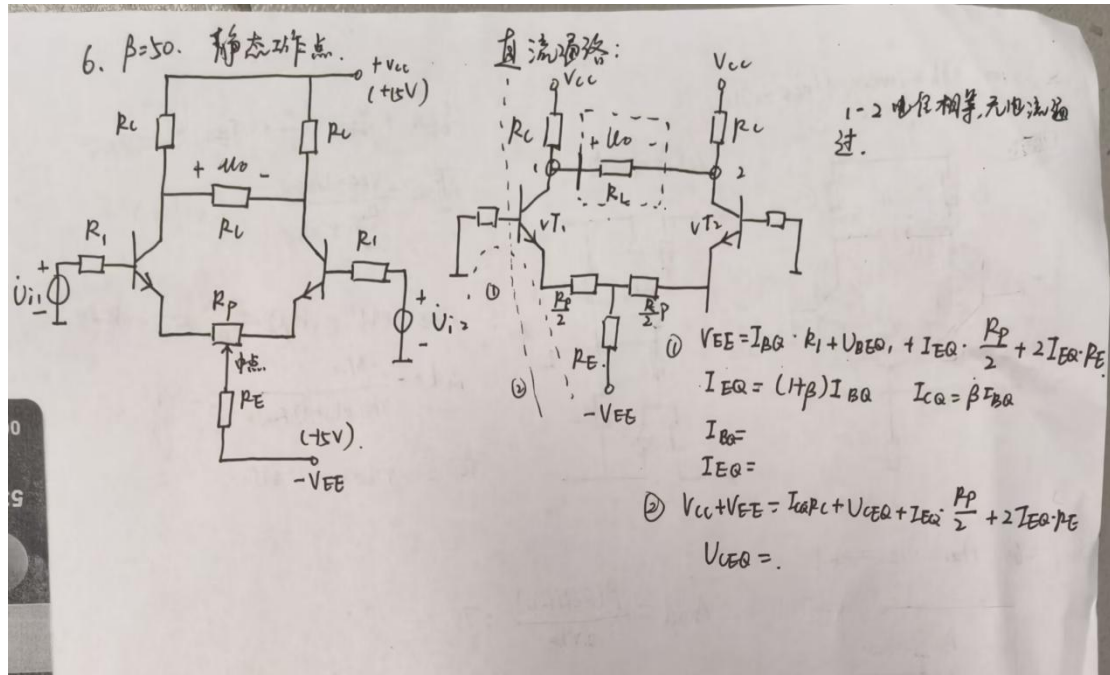
$$U_{CEQ2} = V_{cc} - \beta_2 I_{BQ2} R_{c2} - (1 + \beta_2) I_{BQ2} \cdot R_{e2} = \dots$$



	共射放大电路	共集放大电路
电路结构		
电压放大倍数	$A_u = -\frac{\beta R'_L}{r_{be} + (1+\beta)R_e}$	$A_u = \frac{(1+\beta)R'_L}{r_{be} + (1+\beta)R'_L}$
电流放大倍数	$A_i \approx \beta$	$A_i \approx 1+\beta$
输入、输出电压相位关系	反相	同相
输入电阻	$R_i = R_{b1} // R_{b2} // [r_{be} + (1+\beta)R_e]$	$R_i = R_b // r_{be} + (1+\beta)R'_L$
输出电阻	$R_o = R_c$	$R_o = R_E // \frac{r_{be} + R'_s}{1+\beta} \approx \frac{r_{be} + R'_s}{1+\beta}$