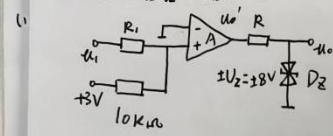


Home work 12.

1. 单限比较器电路:




当 $U_1 > U_T$ 时, $U_P > U_N$, 即 $u_o' = +U_{om}$, $u_o = U_{om} = +U_Z$.
 当 $U_1 < U_T$ 时, $U_P < U_N$, 即 $u_o' = -U_{om}$, $u_o = U_{om} = -U_Z$.
 $u_o = \pm U_Z = \pm 3V$


令 $u_P = u_N$ 得 $U_1 = -3V = U_T$.

$$U_P = \frac{R_1}{R_1 + R_2} U_1 + \frac{R_1}{R_1 + R_2} \times 3V$$

即电压传输特性如图示:

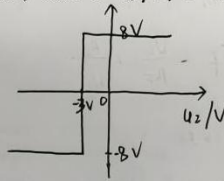


2. 滞回比较器.

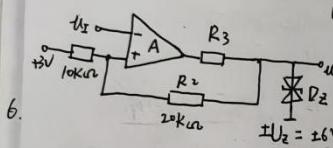


$U_1 < -U_T$, $U_N < U_P$, $u_o = +U_Z$, $u_P = +U_T$
 限幅: $u_o = \pm U_Z = \pm 6V$.
 即电压传输特性如下图所示:

$$U_P = \frac{R_1}{R_1 + R_2} u_o + \frac{R_2}{R_1 + R_2} U_{REF} = U_N = U_1$$






即 $U_{T1} = 0V$, $U_{T2} = 4V$.

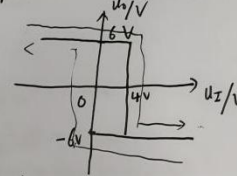

3. 窗口比较器.

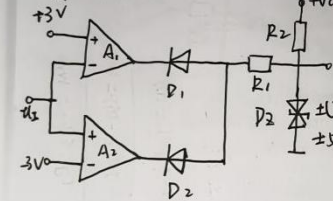


$u_o = \pm U_Z = \pm 5V$
 $\pm U_T = \pm 3V$
 传输特性:

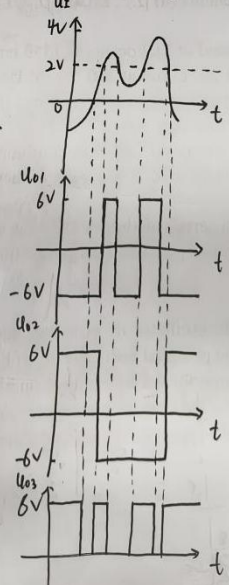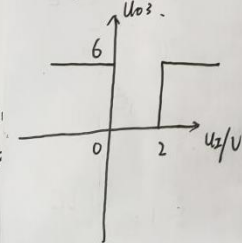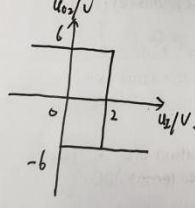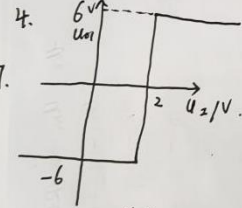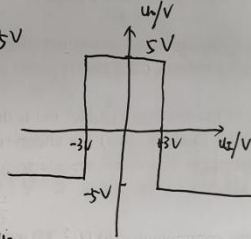

Homework 12.

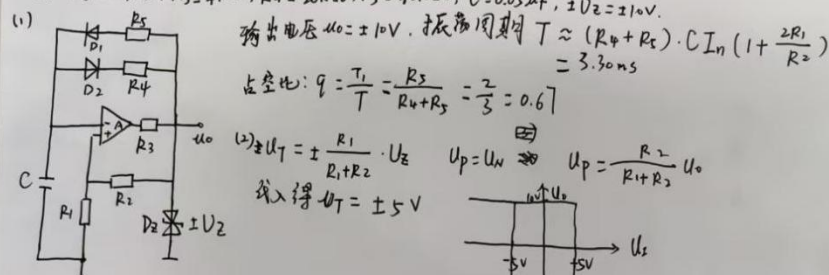
5. $R_1 = R_2 = 20k\Omega$, $R_3 = 4k\Omega$, $R_4 = 20k\Omega$, $R_5 = 40k\Omega$, $C = 0.05\mu F$, $\pm U_Z = \pm 10V$.




输出电压 $u_o = \pm 10V$. 振荡周期 $T \approx (R_4 + R_5) \cdot C \cdot I_n (1 + \frac{2R_1}{R_2})$
 $= 3.30ms$

占空比: $q = \frac{T_1}{T} = \frac{R_5}{R_4 + R_5} = \frac{2}{3} = 0.67$

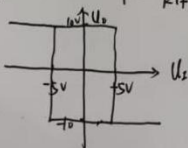(2) $\pm U_T = \pm \frac{R_1}{R_1 + R_2} \cdot U_Z$ $U_p = U_n$ $U_p = \frac{R_2}{R_1 + R_2} u_o$
 代入得 $U_T = \pm 5V$



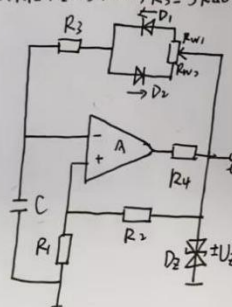6. $R_1 = R_2 = 75k\Omega$, $R_3 = 5k\Omega$, $R_W = 100k\Omega$, $C = 0.1\mu F$, $\pm U_Z = \pm 8V$.



(1) 输出电压 $u_o = \pm 8V$, 振荡周期.

$T \approx (R_W + 2R_3) C I_n (1 + \frac{2R_1}{R_2})$
 $= 12.1ms$

振荡频率: $f = \frac{1}{T} \approx 83Hz$


(2) 当 R_W 为最小值时, 可得 q_{min} .

$q_{min} = \frac{T_1}{T} \approx \frac{R_{W1} + R_3}{R_W + R_3} = \frac{5}{100 + 10} \approx 0.045$


将 R_W 为最大值 $100k\Omega$ 代入, 可得 q_{max} .

$q_{max} = \frac{T_1}{T} \approx \frac{R_{W2} + R_3}{R_W + R_3} = \frac{100 + 5}{100 + 10} \approx 0.95$

即占空比 $T_1/T \approx 0.45 \sim 0.95$.

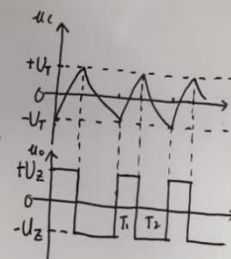


7.

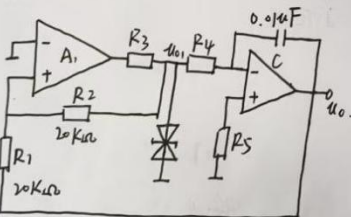

(1) A_1 : 滞回比较器 A_2 : 积分运算电路.


(2) $u_{p1} = \frac{R_1}{R_1 + R_2} \cdot u_{o1} + \frac{R_2}{R_1 + R_2} \cdot u_o = \frac{1}{2}(u_{o1} + u_o)$ $u_{n1} = 0$

解: $\pm U_T = \pm 8V$; 即交变曲线:

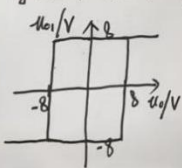

(3) $u_o = \frac{1}{R_4 C} u_{o1} (t_2 - t_1) + u_o(t_1)$

$= -2000 u_{o1} (t_2 - t_1) + u_o(t_1)$

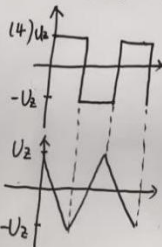

(5) 提高振荡频率, 可以减小 R_4, C, R_1 或增加 R_2 .

$T = \frac{4R_1 R_4 C}{R_2}$