
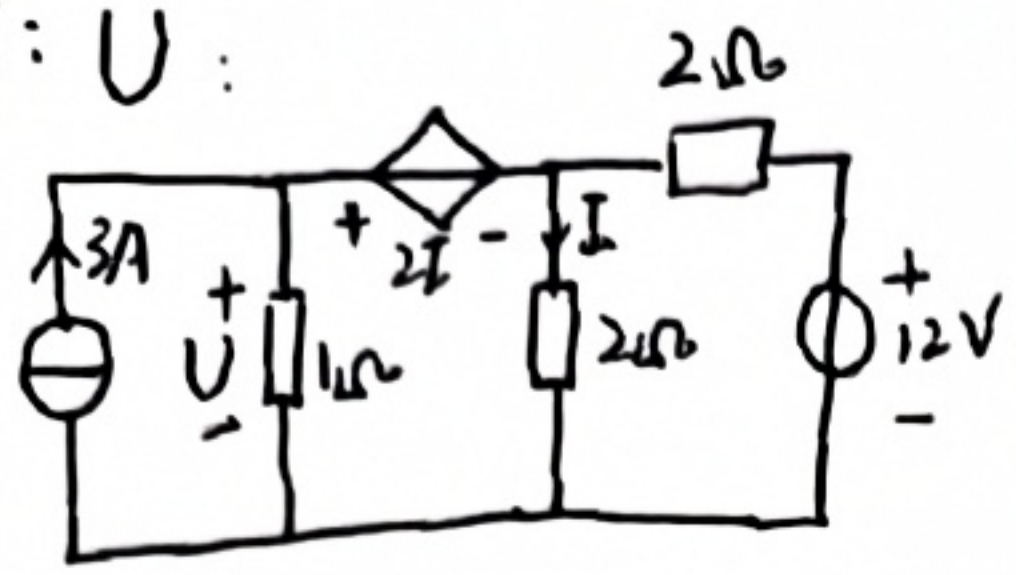


3月30日作业： 作业②

1. 叠加定理求 U :

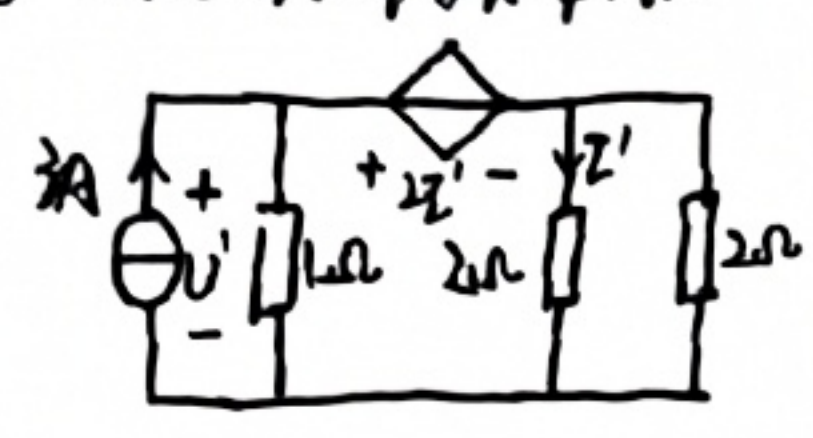


① 3A 电源单独作用




1Ω 电阻上 U'
 $U' = 2I' + 2I'$
 $\frac{U'}{1} + 2I' = 3$ 即 $U' = 2V, I' = 0.5A$

② 12V 电源

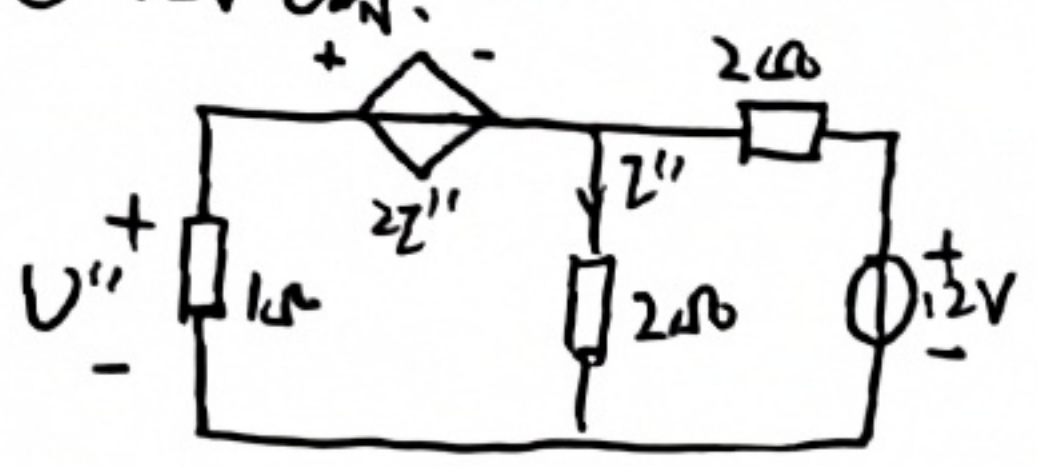

$U'' = 2I' + 2I''$
 $2I'' = -2 \times (I'' + U'') + 12$
 即 $U'' = 4V, I'' = 1A$
 故 $U^* = U' + U'' = 6V$


2. 戴维南等效电路

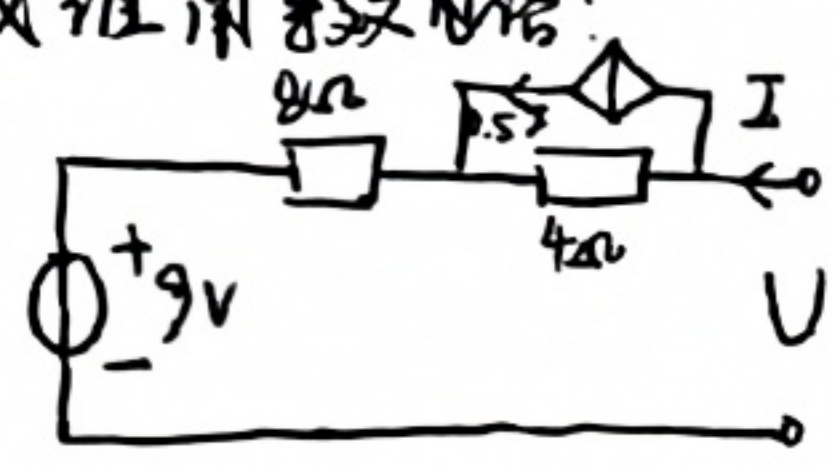



$U = 4 \times (I - 0.5I) + 8I$
 $R_0 = \frac{U}{I} = 10\Omega$

开路电压：当端开路时， $I = 0$ 即无控源 $0.5I = 0$ 。
 因此电路中只有 9V 电压源作用。
 即 $U_{oc} = 9V$

即等效电路为：

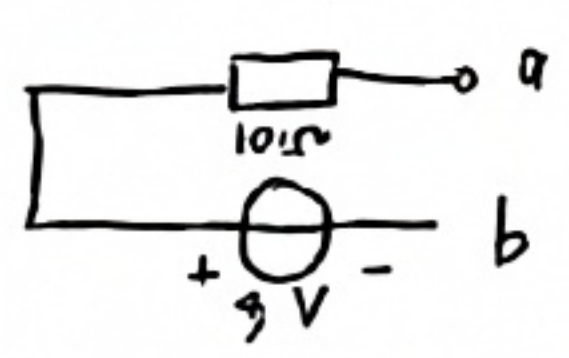

3. 从 ab 端看入的等效电阻

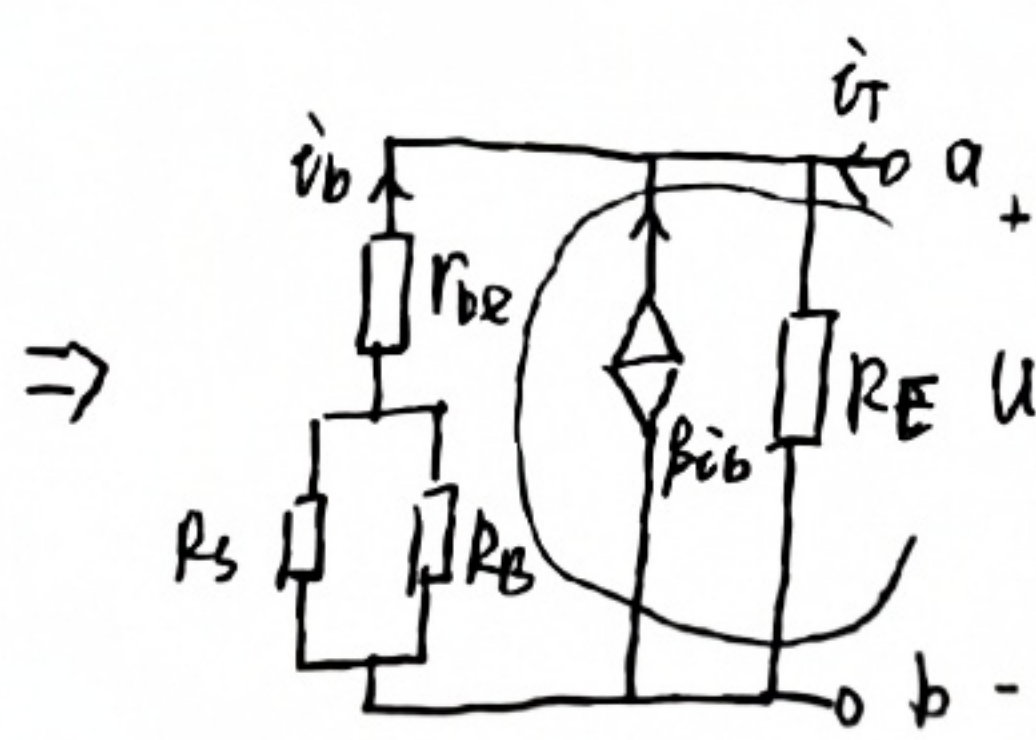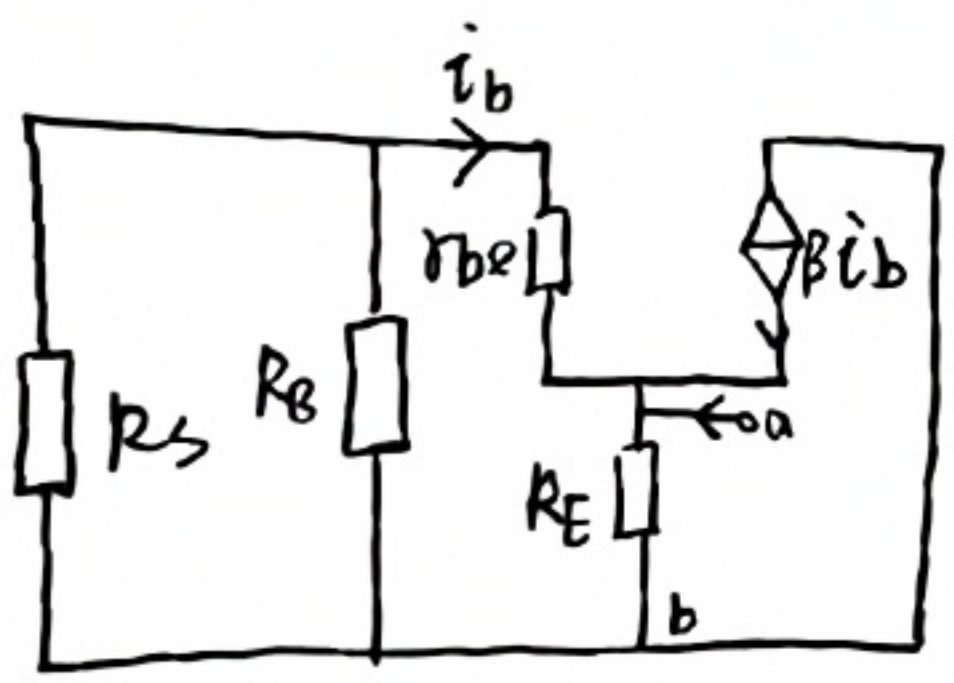

假设 i_T 电流方向：
 流过 R_E 的电流为： $i_E = i_T + i_b + \beta i_b$
 $U_T = R_E \cdot i_E$
 回路： $(R_s \parallel R_B + r_{be}) i_b + U_T = 0$
 $\Rightarrow U_T = \frac{(R_s \parallel R_B + r_{be}) R_E}{R_s \parallel R_B + r_{be} + (1 + \beta) R_E} \cdot i_T$
 $Y_{ab} = \frac{U_T}{i_T} = \frac{(R_s \parallel R_B + r_{be}) R_E}{R_s \parallel R_B + r_{be} + (1 + \beta) R_E}$